
1.

BPLC pixel circuit (IEEE/OSA JDT 2015)

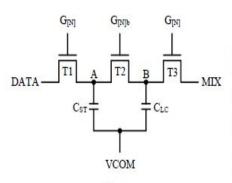

$$V_A = V_{LC} = \frac{1}{2} \left(V_{DATA} + V_{MIX} \right)$$

Simulate three conditions and save your waveforms of node A and node B. Please explain the voltage change of node A and B.

=> Enlarge V_{LC} from $\pm 15~V$ to $\pm 20~V$

Simulated parameter:

$$C_{LC} = 6 pF$$

$$C_{ST} = 6 pF$$

$$M_{T1,T2} = 100$$

$$M_{T3} = 300$$

$$VCOM = 0 V$$

Initial
$$V_A = V_B = 0 V$$

Simulated condition:


(1) For
$$MIX = 0 V$$


$$V_{DATA} = 0 V$$

(2) For MIX = 10 V
$$V_{DATA} = 7.5 V$$


(3) For MIX =
$$25 \text{ V}$$

$$V_{DATA} = 15 \text{ V}$$

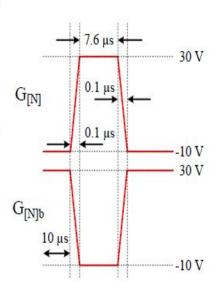


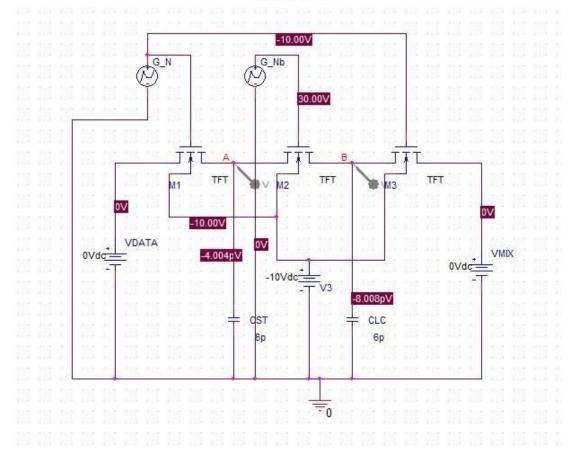


Condition 1:

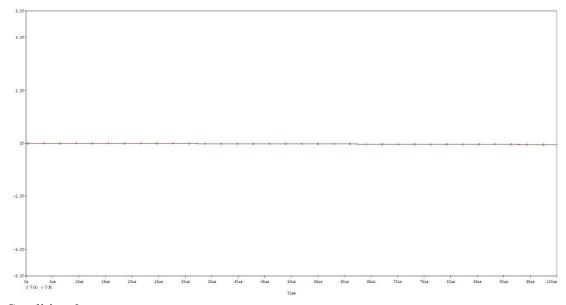

Condition 2:

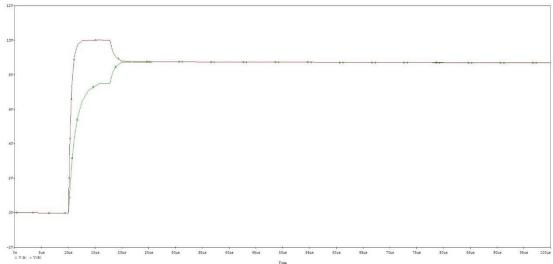

Condition 3:

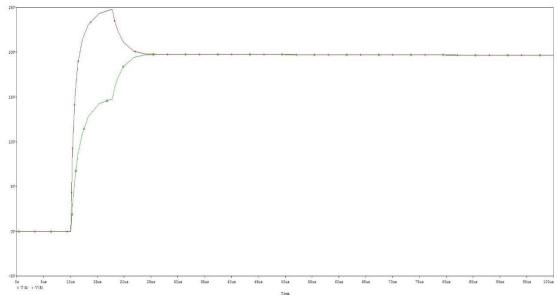


Please explain the voltage change of node A and B.

$$V_{A} = V_{B} = 1/2 * (V_{DATA} + V_{MIX})$$


 $V_A = V_B = 1/2*(V_{DATA} + V_{MIX})$ 可看出 $V_{MIX} + V_{DATA}$ 值增加,實際值與理論值差距也增加,發生此結果可能是電容漏電或者其他因素的影響。

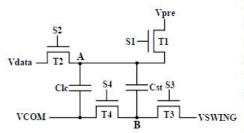2.

BPLC pixel circuit (IDW 2013) => Enlarge V_{LC} from $\pm 15 \text{ V}$ to $\pm 20 \text{ V}$



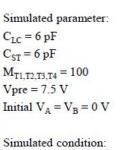
* Simulate normal mode and coupling mode under positive polarity, and save your waveforms of node A and node B. Please explain the voltage change of node A and B.




(1) For VCOM = 0 V
VSWING = 0 V


$$V_{DATA} = 15 \text{ V}$$

(2) For VCOM = 0 VVSWING = -10 V $V_{DATA} = 15 \text{ V}$

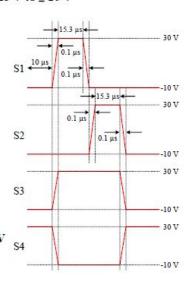


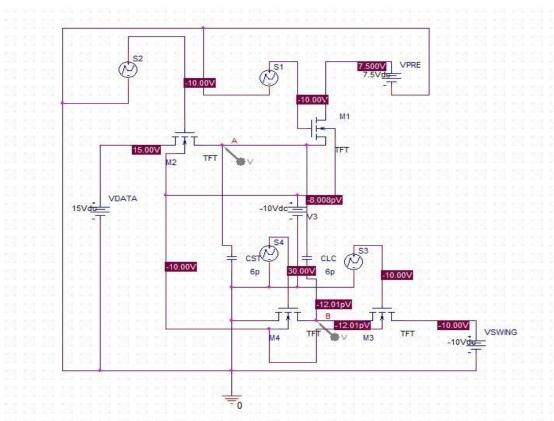

Condition 1:

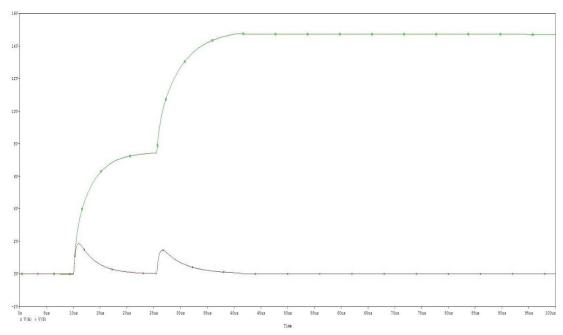

Condition 2:

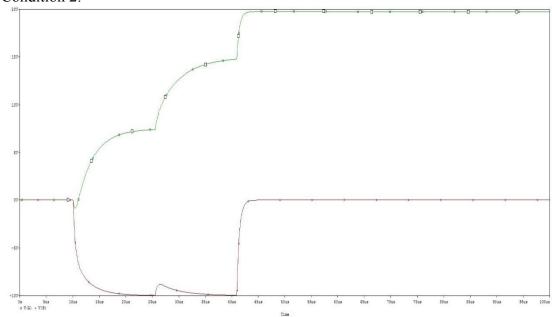

Please explain the voltage change of node A and B.

Ans:

Condition 1:


T1打開對A點灌入7.5V,T2打開對A點灌入15V的電壓,灌入電壓的同時,B 點受A點影響,電壓略為上升,但因VSWING影響而拉回0V。


Condition 2:

在A點灌入7.5V的同時,B點拉至-10V,A點受B點影響被拉低一點後才開始上升,41us時,T4打開,B點灌入VCOM拉回0V。

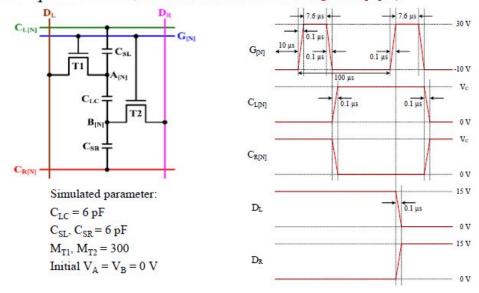
3. Pixel operation

BPLC pixel circuit (IEEE EDL 2015 & SID 2015 distinguished paper)



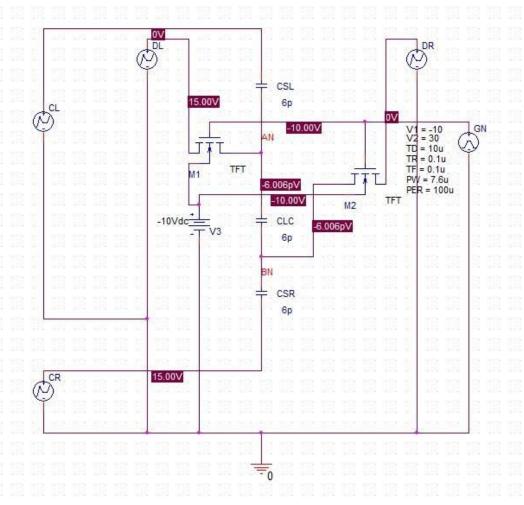

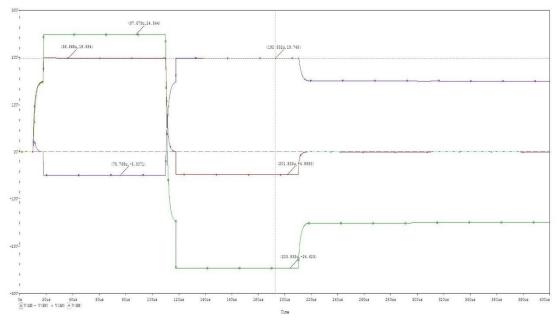I. Please design the value of $V_{\rm C}$ to achieve the maximum $V_{\rm LC}(A[N]-B[N])$ of 25 V and -25 V.




Ans:

$$V_{LC} = V_{DL} - V_{DR} \pm (2/3) * V_{C}$$

因此推得 $V_{C} = 15V$

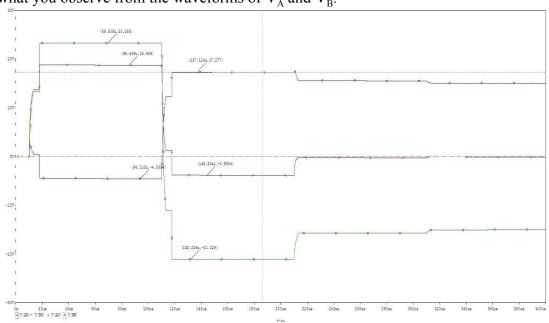
II. If the pulse-width of G[N]is shortened from 7.6 μ s to 3.3 μ s, please explain what you observe from the waveforms of V_A and V_B .



Ans:

觀察可知充放電曲線有一段為平直線,由於充放電時間不足,因此 $V_{
m LC}$ 低於前一模擬。

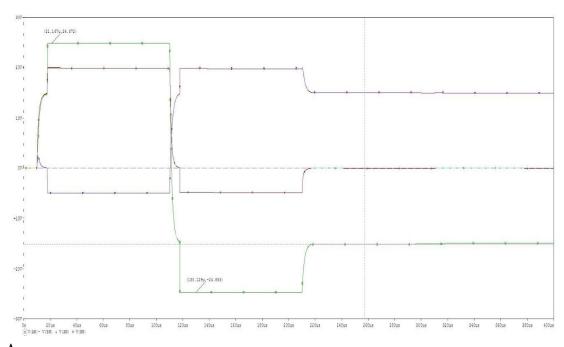III. How to adjust problem 2 to achieve the result in problem 1?



Ans: 調整TFT的M值到800左右可得到與第一題相近的結果。