
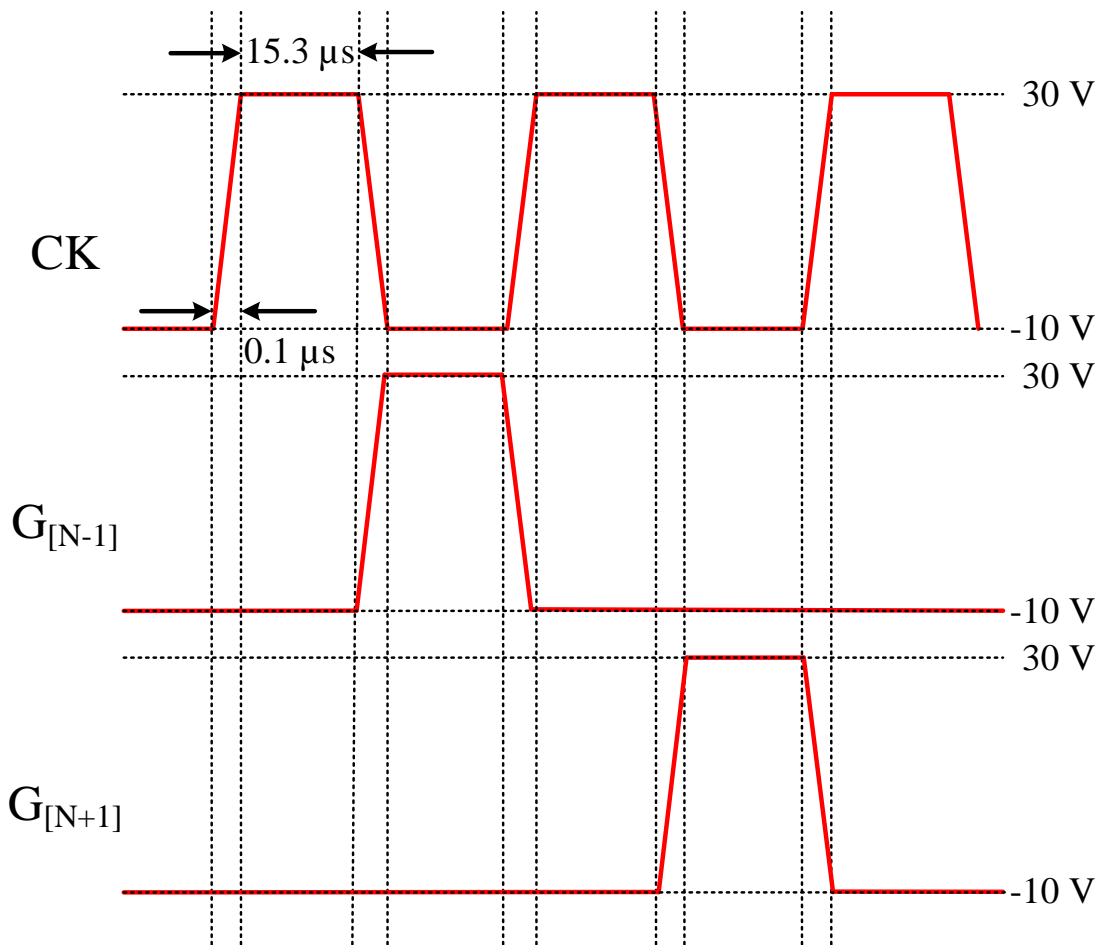


TFT LCD Simulation

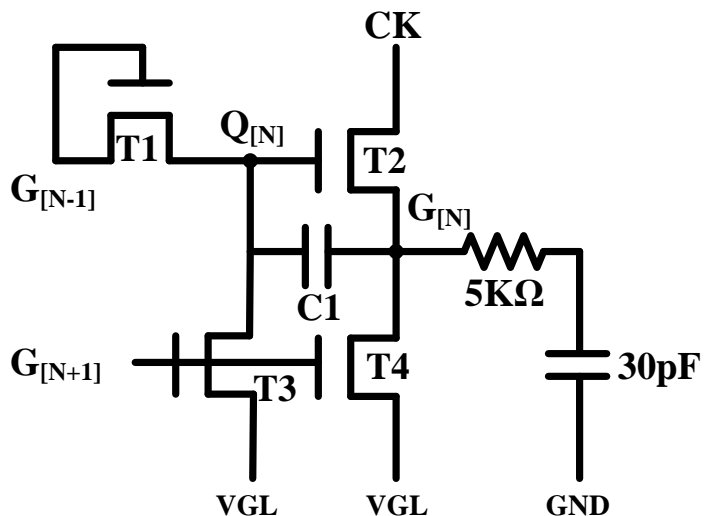

1. Dynamic Shift Register (Single-type MOS device)






Simulated parameter:

$V_{GL} = -10 \text{ V}$ $C1 = 2 \text{ pF}$

$M_{T1} = 50$ $M_{T3} = 50$

$M_{T2} = 300$ $M_{T4} = 300$


TFT LCD Simulation

-  i. Please explain how the shift register generates the high level of $G_{[N]}$. (Hint: investigate $Q_{[N]}$ waveform)
-  ii. Please record the rising time and falling time of $G_{[N]}$.
-  iii. Change M_{T2} and M_{T4} to 500, and record the rising time and falling time of $G_{[N]}$ again. What's the difference from question ii, and why?

TFT LCD Simulation



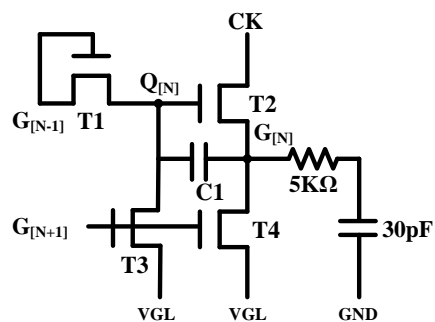2. Dynamic Shift Register (Two-stage operation)





Simulated parameter:


$V_{GL} = -10\text{ V}$ $C1 = 2\text{ pF}$


$M_{T1} = 50$ $M_{T3} = 50$

$M_{T2} = 300$ $M_{T4} = 300$

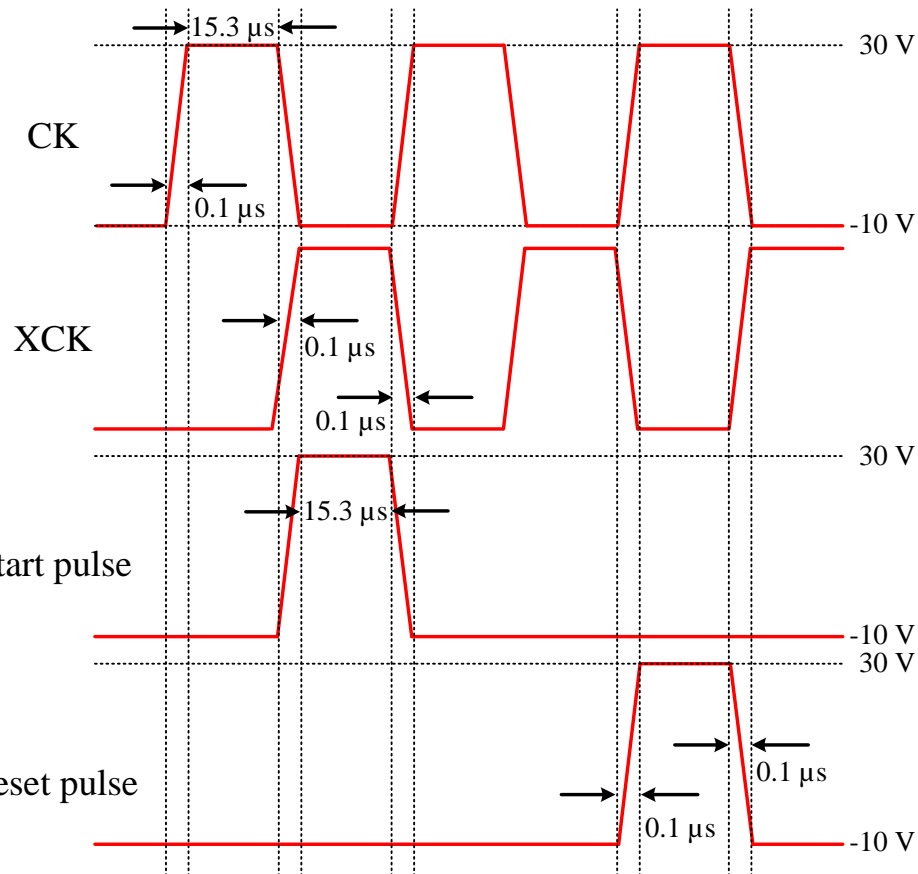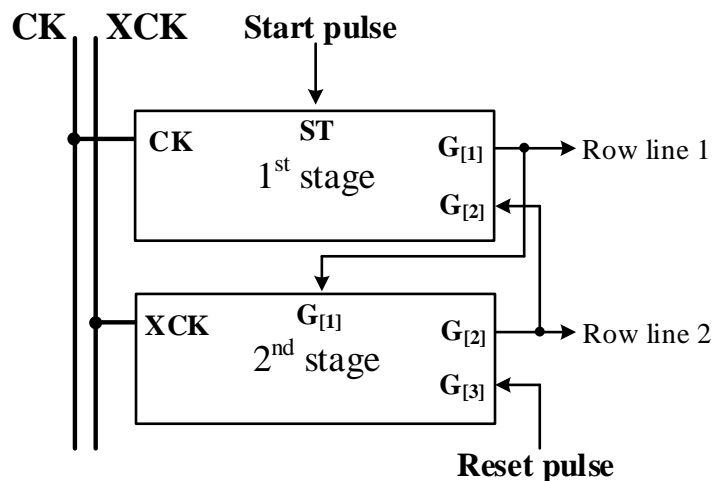

TFT LCD Simulation

-  i. Please save the sequential output waveforms of two stages.
($G_{[1]}$ and $G_{[2]}$)

-  ii. What are the functions of “start pulse” and “reset pulse”?